

# SPEED CONTROLLED DC MOTOR

*by* Gourav D H

---

**Submission date:** 03-May-2020 12:02PM (UTC+0530)

**Submission ID:** 1314443236

**File name:** 1NH18EC039.pdf (846.01K)

**Word count:** 4796

**Character count:** 23057

**“SPEED CONTROLLED DC MOTOR”****A MINI PROJECT****REPORT***Submitted by***GOURAV D H (1NH18EC039)****CHITTE ABHINAY KUMAR REDDY (1NH18EC026)****AVINASH U G (1NH18EC015)****C ROHIT (1NH18EC025)****LIST OF FIGURES**

<b>FIGURE No</b>	<b>FIGURE DESCRIPTION</b>	<b>Page No</b>
1	Circuit diagram	9
2	NE 555 IC	12
3	Diode	13
4	Schottky Diode	22
5	Water pump	24

6	Battery	25
7	Bread board	26

### LIST OF TABLES

SL No	Table No	TABLE DESCRIPTION	Page No
1	1	Components	9
2	2	Pins of 555 Timer	12

2

**ABSTRACT**

The speed control of direct current (DC) motor for various applications is very important. In particular requirement, setting a speed DC motor as the driving equipment must be performed remotely. Under that condition, conducted a research on a DC motor speed control with pulse width modulation (PWM) method of the infrared remote control. PWM is method that may be used as an efficient DC motor speed control.

9

Pulse width modulation (PWM), or pulse-duration modulation (PDM), is a method of reducing the average power delivered by an electrical signal, by effectively chopping it up into discrete parts. The average value of voltage (and current) fed to the load is controlled by turning the switch between supply and load on and off at a fast rate.

PWM is particularly suited for running inertial loads such as motors, which are not as easily affected by this discrete switching, because they have inertia to react slow. The PWM switching frequency has to be high enough not to affect the load, which is to say that the resultant waveform perceived by the load must be as smooth as possible.

## CHAPTER 1

### INTRODUCTION

Today's industries are increasingly demanding process automation in all sectors. Automation results into better quality, increased production and reduced costs. The variable speed drives, which can control the speed of A.C/D.C motors, are indispensable controlling elements in automation systems. Depending on the applications, some of them are fixed speed and some of the variable speed drives.

The variable speed drives, till a couple of decades back, had various limitations, such as poor efficiencies, larger space, lower speeds, etc., However, the advent of power electronic devices such as power MOSFETs, IGBTs etc., and today we have variable speed drive systems which are not only smaller in size but also very efficient, highly reliable and meeting all the stringent demands of various industries of modern era.

Direct currents (DC) motors have been used in variable speed drives for a long time. The versatile characteristics of dc motors can provide high starting torques which is required for traction drives. Control over a wide speed range, both below and above the rated speed can be very easily achieved. The methods of speed control are simpler and less expensive than those of alternating current motors.

There are different techniques available for the speed control of DC motors. The phase control method is widely adopted in which ac to dc converters are used to supply the dc motors, but has certain limitations mainly it generates harmonics on the power line and it also has poor p.f. when operated at lower speeds. The second method is pwm technique, which has got better advantages over the phase control.

## CHAPTER 2

### LITERATURE SURVEY

<sup>4</sup> The DC motors are in general much more adaptable speed drives than AC motors which are associated with a constant speed rotating field. Indeed one of the primary reasons for the strong competitive position of DC motors in modern industrial drives is the wide range of specified afforded we know the equation

$$N = K \left( \frac{V - I_a R_a}{\Phi} \right)$$

$$= K \left( \frac{V - I_a R_a}{\Phi} \right)$$

Where V=supply voltage (volts)<sup>23</sup>

$I_a$  = armature current (amps)

$R_a$ =armature resistance (ohms)

$\Phi$ =flux per pole (Weber)

This equation gives two methods of effective speed changes i.e.

- a) The variation of field excitation, if this causes in the flux per pole  $\Phi$  and is known as the field control.
- b) The variation of terminal voltage (V).this method is known as armature control.

**a) FLUX CONTROL METHOD:**

It is known that  $N \propto 1/\Phi$  by decreasing the flux, thus speed can be increased and vice versa. Hence, name flux or field control method.

The flux of DC motor can be changed by changing with help of a shunt field rheostat. Since in relatively small, shunt field rheostat has to carry only a small, so that rheostat is small in size. This method therefore very efficient in non-interpolar machines the speed can be increased by this method in the ratio 2:1 any further weakening of flux  $\Phi$  adversely affect the communication

And hence puts a limit to the maximum speed obtainable with this method in machines fitted with interlopes in ratio of maximum to minimum speeds of 6:1 is fairly common.

**b) ARMATURE OR RHEOSTAT CONTROL METHOD:**

This method is used when speeds below the no load speed are required. As the supply voltage is normally constant, the voltage across the armature is varied by inserting a variable rheostat or controller resistance in series with the armature circuit as shown in fig1.3 as controller resistance is increased, potential difference across the armature is decreased, thereby decreasing the armature speed. For a load of constant torque, speed is approximately proportional to the potential difference.

## CHAPTER 3

### PROPOSED METHODOLOGY

In our proposed project, a 5 H.P DC shunt motor circuitry is designed, and developed using pulse with modulation (PWM).The pulse width modulation can be achieved in several ways. In the present project, the PWM generation is done using timer IC.

5 In order to have better open loop speed control as demand varies frequently like in traction system and many operations in industry must be control manually, PWM is most efficient and cheap speed control method for dc drives. By varying resistor pot only we can control the speed of motor states that simple and easy method.

Fig 1

## CHAPTER 3.1

### COMPONENTS REQUIRED

S.No.	Required Components	Remarks	Quantity
1	IC's	NE555	1
2	Transistor	IRF540 MOSFET	1
3	Diode	1NH4001	1
		1N5819	2
4	Water pump	3-6 V 80-120 L/H	1



		DC Magnetic driving	
5	Resistor	Quarter watt	10k ohm - 3 100k Ohm(POT) – 1
6	Capacitor	Ceramic	100nF – 1 100pF - 1

## CHAPTER 4

### PROJECT DESCRIPTION

Pin 1 of 555 is connected to GND. Pins 8 and 4 are connected to +12V Supply.

Pins 6 and 2 are short and a 100nF Capacitor is connected between Pin 2 and GND. The wiper pin of the POT is connected to Pin 3 of 555. Two Schottky diodes (1N5819) are connected to the other two pins of the POT as shown in the circuit diagram.

The common point of the diodes is connected to Pin 2. Pin 7 is pulled high with the help of a 10K $\Omega$  Resistor. The Gate terminal of the MOSFET is connected to Pin 7 of 555. The motor is

connected between +12V Supply and Drain of MOSFET while the Source of MOSFET is connected to GND.

A PN Junction Diode is connected across the Motor terminals to prevent the back emf.

In this circuit, the DC motor is operated by a 555 integrated circuit. The IC 555 in this circuit is being operated in astable mode, which produces a continuous HIGH and LOW pulses.

In this mode, the 555 IC can be used as a pulse width modulator with a few small adjustments to the circuit. The frequency of operation of the circuit is provided by the passive parameters of resistances and capacitors attached to it.

## **CHAPTER 4.1**

### **HARDWARE DESCRIPTION**

#### **NE555 IC pin diagram :**

This IC contains an SR flip flop as shown in the figure

Fig 2

### Some important features of the 555 timer:

555 timer is used in almost every electronic circuit today. For a 555 timer working as a flip flop or as a multi-vibrator, it has a particular set of configurations. Some of the major features of the 555 timer would be,

- It operates from a wide range of power ranging from +5 Volts to +18 Volts supply voltage.
- Sinking or sourcing 200 mA of load current.
- The external components should be selected properly so that the timing intervals can be made into several minutes along with the frequencies exceeding several hundred kilohertz.
- The output of a 555 timer can drive a transistor-transistor logic (TTL) due to its high current output.
- It has a temperature stability of 50 parts per million (ppm) per degree Celsius change in temperature which is equivalent to 0.005 %/ °C.
- The duty cycle of the timer is adjustable.
- Also, the maximum power dissipation per package is 600 mW and its trigger and reset inputs has logic compatibility.

## Pin diagram and description

Pin	Name	Purpose
1	GND	Ground reference voltage, low level (0 V)
2	TRIG	The OUT pin goes high and a timing interval starts when this input falls below $1/2$ of CTRL voltage (which is typically $1/3 V_{cc}$ , CTRL being $2/3 V_{cc}$ by default if CTRL is left open). In other words, OUT is high as long as the trigger low. Output of the timer totally depends upon the amplitude of the external trigger voltage applied to this pin.
3	OUT	This output is driven to approximately 1.7 V below $+V_{cc}$ , or to GND.
4	RESET	A timing interval may be reset by driving this input to GND, but the timing does not begin again until RESET rises above approximately 0.7 volts. Overrides TRIG which overrides threshold.
5	CTRL	Provides “control” access to the internal voltage divider (by default, $2/3 V_{cc}$ ).
6	THR	The timing (OUT high) interval ends when the voltage at threshold is greater than that at CTRL ( $2/3 V_{cc}$ if CTRL is open).
7	DIS	Open collector output which may discharge a capacitor between intervals. In phase with output.

8	Vcc	Positive supply voltage, which is usually between 3 and 15 V depending is variable
---	-----	--

The timer IC 555 was introduced around 1971 by the company Signetics under the name SE555 / NE555 and was called "The Time Machine IC". It offered circuit designers a relatively inexpensive, stable and easy-to-use integrated circuit for monostable and astable applications. Since this device was first marketed, many unique and innovative circuits have been developed and presented in various commercial, professional and leisure publications. Over the past decade, some manufacturers have stopped making these timers for reasons of competition or other reasons. However, other companies, such as NTE (a sub-division of Philips) have resumed their activities where some have left.

Although the CMOS version of this IC, such as the Motorola MC1455, is primarily used, the standard type is still available, but many enhancements and variations have been made to the circuits. But all types are compatible with pin plugs. In this tutorial, the 555 timer is examined in detail, as are its uses, either alone or in combination with other semiconductor devices. This timer uses a labyrinth of transistors, diodes and resistors and, for this complex reason, a more simplified (but precise) block diagram is used to explain the internal organization of 555. The 555, in fig. 1 and FIG. 2 above, is available in two cases, either the round metal housing called "T", or the 8-pin DIP housing better known, "V". About 20 years ago, the type of canister was almost standard (SE / NE types). The 556 timer is a 555 dual version and comes in a 14-pin DIP package, the 558 is a quad version with four 555s also in a 14-pin DIP package.

**Pin 1 (ground):** The ground (or common) pin is the most negative power potential of the device, which is normally connected to the common (ground) circuit when operating from positive supply voltages.

**Pin 2 (trigger):** This pin is the input of the lower comparator and is used to adjust the latch, which makes the output high. This is the beginning of the time sequence in the monostable operation. The shot is obtained by taking the pin up and down with a voltage of  $\frac{1}{3} V_+$  (or, in general, half of the voltage appearing on pin 5). The action of the activation input is level sensitive, allowing the use of slow change rate waveforms, as well as pulses, as activation sources. The trigger pulse must be shorter than the time interval determined by external R & C. If this pin remains low longer, the output will remain high until the trigger input increases again. A caution to observe with the trigger input signal is that it should not be less than  $\frac{1}{3} V_+$  for a longer period than the synchronization cycle. If allowed, the timer will be reactivated at the end of the first output pulse. Therefore, when the timer is used in monostable mode with input pulses longer than the desired output pulse width, the input trigger must be effectively shortened by differentiation. The minimum pulse width allowed for activation depends to some extent on the pulse level, but in general if greater than  $1\mu\text{s}$  (micro-second), the activation will be reliable. A second precaution concerning the trigger input refers to the storage duration in the lower comparator. This part of the circuit may have normal stopping delays of several microseconds after activation; that is, the lock may still have an activation input during this period after the activation pulse. In practice, this means that the minimum monostable output pulse width must be of the order of  $10\mu\text{s}$  in order to avoid possible double activation due to this effect. The voltage range that can safely be applied to the trip pin is between  $V_+$  and ground. A DC current, called the tripping current, must also flow from this terminal to the external circuit. This current is usually  $500\text{nA}$  (nano-amp) and will set the upper limit of allowable resistance of pin 2 to earth. For an astable configuration operating at  $V_+ = 5\text{ volts}$ , this resistance is  $3\text{ megaohms}$ ; It can be higher for a higher level of  $V_+$ .

**Pin 3 (output):** output 555 is from a high current totem stage consisting of transistors Q20 to Q24. Transistors Q21 and Q22 provide a drive for source-type loads, and their Darlington connection provides a high output voltage of about 1.7 volts less than the  $V +$  power level used. Transistor Q24 offers the possibility of absorbing the current for low state loads called  $V +$  (as typical TTL inputs). The transistor Q24 has a low saturation voltage, which allows it to interact directly with a good noise margin when it performs the current reduction logic. However, the exact output saturation levels vary considerably with the supply voltage, for both high and low states. At a  $V +$  of 5 volts, for example, the low state  $V_{ce}(\text{sat})$  is typically 0.25 volts at 5 mA. However, when running at 15 volts, it can absorb 200 mA if a 2 volt output voltage level is allowed (the power dissipation must be taken into account in this case, of course). The high state level is typically 3.3 volts at  $V + = 5$  volts; 13.3 volts at  $V + = 15$  volts. The rise and fall times of the output waveform are quite fast, the typical switching times are 100nS. The state of the output pin will always reflect the opposite of the logic state of the latch, which can be seen by examining FIG. 3. Since the lock itself is not directly accessible, this relation can be better explained in terms of the activation activation lock conditions. To activate the output in the high state, the activation input is momentarily taken from a higher level to a lower level. [see "Pin 2 - Trigger"]. This causes locking and high output. The performance of the lower comparator is the only way to set the output high. The output can return to a low state by raising the threshold from a lower level to a higher level [see "Pin 6 - Threshold"], which resets the latch. The output can also be reduced by bringing the reset to a low state near the ground [see "Pin 4 - Reset"]. The output voltage available on this pin is approximately equal to the  $V_{cc}$  applied to pin 8 minus 1.7Vs.

**Pin 4 (reset):** This pin is also used to reset the latch and return the output to a low state. The threshold level of the reset voltage is 0.7 volts and a 0.1 mA dissipation current of this pin is required to restart the device. These levels are relatively independent of the  $V +$  level of operation; Thus, the reset input is compatible with TTL for any supply voltage. The reset input is a primary function. that is, it will force the output to a low state regardless of the state of the other inputs. Therefore, it can be used to prematurely terminate an output pulse, to block oscillations from "on" to "off", etc. The delay time between the restart and the output is generally



of the order of  $0.5 \mu\text{s}$  and the minimum width of the reset pulse is  $0.5 \mu\text{s}$ . However, none of these numbers are guaranteed and may vary from manufacturer to manufacturer. In summary, the reset pin is used to reset the latch that controls the state of output pin 3. The pin is activated when a voltage level between 0 and 0.4 volts is applied to the pin. The reset pin will force the output to a low level, regardless of the state in which the other inputs of the flip-flop are located. When not in use, it is recommended to connect the reset input to  $V +$  in order to avoid the possibility of false restart.

**Pin 5 (control voltage):** This pin allows direct access to the  $2/3 V +$  voltage division point, the reference level of the upper comparator. It also allows indirect access to the lower comparator because there is a 2: 1 splitter (R8 - R9) from this point to the lower comparator reference input, Q13. The use of this terminal is a user option, but it allows extreme flexibility by allowing the modification of the period, the restart of the comparator, etc. When timer 555 is used in a voltage controlled mode, its voltage operation varies from about 1 volt less than  $V +$  to 2 volts of mass (although this is not guaranteed). Voltages may safely be applied outside these limits, but must be limited within the  $V +$  and ground limits for reasons of reliability. By applying a voltage to this pin, it is possible to vary the duration of the device independently of the RC network. The control voltage can vary from 45 to 90% of the  $V_{cc}$  in monostable mode, which allows the output pulse width to be controlled independently of RC. When used in astable mode, the control voltage can vary from 1.7 V to full VDC. Variable voltage in astable mode will produce a modulated frequency (FM) output. If the control voltage pin is not used, it is recommended to ground it with a capacitor of about  $0.01\mu\text{F}$  ( $10\text{nF}$ ) for noise immunity because it is an input comparison. This fact is not evident in many 555 circuits since I have seen many circuits with "no-pin-5" connected to anything, but this is the proper procedure. The small ceramic lid can eliminate false activations.

**Pin 6 (threshold):** Pin 6 is an input of the upper comparator (the other is pin 5) and is used to reset the latch, resulting in low output. The reset through this terminal is made by taking the bottom terminal to a voltage of  $2/3 V +$  (the normal voltage on pin 5). The action of the threshold pin is level sensitive, which allows slow rate of change waveforms. The voltage range that can



safely be applied to the threshold pin is between  $V +$  and ground. A direct current, called the current threshold, must also reach this terminal from the external circuit. This current is generally  $0.1 \mu\text{A}$  and will define the upper limit of total resistance allowed from pin 6 to  $V +$ . For any synchronization setting that operates at  $V + = 5$  volts, this resistance is  $16 \text{ M}\Omega$ . For operation at 15 volts, the maximum resistance value is  $20 \text{ M}\Omega$ .

**Pin 7 (discharge):** this pin is connected to the open collector of an NPN transistor (Q14), whose emitter is grounded, so that when the transistor is activated, pin 7 is actually short-circuited to the mass. Generally, the sync capacitor is connected between pin 7 and ground and is discharged when the transistor is turned on. The state of attack of this transistor has a synchronization identical to that of the output stage. It is "on" (low resistance to earth) when the output is low and "off" (high resistance to earth) when the output is high. In the monostable and astable time modes, this transistor switch is used to ground the appropriate nodes of the synchronization network. The saturation voltage is generally less than  $100 \text{ mV}$  (millivolts) for currents of  $5 \text{ mA}$  or less, and the leakage in the off state is approximately  $20 \text{ nA}$  (however, these parameters are not specified by all manufacturers). The maximum collector current is internally limited by design, thus eliminating capacitor size restrictions due to the maximum discharge of the pulse current. In some applications, this open-collector output can be used as an auxiliary output terminal, with a current-dissipating capacity similar to that of the output (pin 3).

**Pin 8 ( $V +$ ):** Pin  $V +$  (also called  $V_{cc}$ ) is the positive power supply terminal of the timer CI 555. The operating voltage supply range of the 555 is between  $+4.5$  volts (minimum) and  $+16$  volts (maximum). It is specified for operation between  $+5$  volts and  $+15$  volts. The device will operate essentially in the same way in this voltage range without changing the period. In fact, the most significant operating difference is the capacity of the output inverter, which increases for both the current and voltage ranges as the supply voltage increases. The sensitivity of the time interval to the variation of the supply voltage is low, typically  $0.1\%$  per volt. There are special and military devices operating at voltages up to  $18 \text{ V}$ .

**Diode:**

**Diode**, an electrical component that allows the flow of current in only one direction. In circuit diagrams, a diode is represented by a triangle with a line across one vertex. The most common type of diode uses a p n junction. In this type of diode, one material ( $n$ ) in which electrons are charge carriers abuts a second material ( $p$ ) in which holes (places depleted of electrons that act as positively charged particles) act as charge carriers. At their interface, a depletion region is

formed across which electrons diffuse to fill holes in the  $p$ -side. This stops the further flow of electrons. When this junction is forward biased (that is, a positive voltage is applied to the  $p$ -side), electrons can easily move across the junction to fill the holes, and a current flows through the diode. When the junction is reverse biased (that is, a negative voltage is applied to the  $p$ -side), the depletion region widens and electrons cannot easily move across. The current remains very small until a certain voltage (the breakdown voltage) is reached and the current suddenly increases.

Fig 3

The Schottky diode, also known as Schottky barrier diode or hot-carrier diode, is a semiconductor diode formed by the junction of a semiconductor with a metal. It has a low forward voltage drop and a very fast switching action. The cat's-whisker detectors used in the early days of wireless and metal rectifiers used in early power applications can be considered primitive Schottky diodes.

When sufficient forward voltage is applied, a current flows in the forward direction. A silicon diode has a typical forward voltage of 600–700 mV, while the Schottky's forward voltage is 150–450 mV. This lower forward voltage requirement allows higher switching speeds and better system efficiency.

Fig 4

## WATER PUMP MOTOR:

Micro DC 3-6V Micro Submersible Pump Mini water pump For Fountain Garden Mini water circulation System DIY project. This is a low cost, small size Submersible Pump Motor which can be operated from a 3 ~ 6V power supply. It can take up to 120 liters per hour with very low current consumption of 220mA. Just connect tube pipe to the motor outlet, submerge it in water and power it. Make sure that the water level is always higher than the motor. Dry run may damage the motor due to heating and it will also produce noise.

### Specifications:-

Operating Voltage : 3 ~ 6V

Operating Current : 130 ~ 220mA

Flow Rate : 80 ~ 120 L/H

Maximum Lift : 40 ~ 110 mm

Continuous Working Life : 500 hours

Driving Mode : DC, Magnetic Driving

Material : Engineering Plastic

Outlet Outside Diameter : 7.5 mm

Outlet Inside Diameter : 5 mm

Fig 5

6

**POWER SUPPLY:**

A power supply is a device that supplies electric power to a electric load .The term is most commonly referred to electric power converts that converts one form of electrical energy to another ,though it may also refer to that convert another form of energy ( mechanical chemical, solar) to electrical energy . The regulated power supply is that controls the output voltage or current to a specific value ;the controlled value is held nearly .

Fig 6

**BREADBOARD:**

A breadboard is a solderless device for temporary prototype with electronics and test circuit designs. Most electronic components in electronic circuits can be interconnected by inserting their leads or terminals into the holes and then making connections through wires where appropriate.

Fig 7

**RESULT**

Under Progress

## **CHAPTER 6**

### **CONCLUSION AND FUTURE SCOPE**

- One of the best things about this circuit is that you can make it work as an astable multivibrator with little hardware and little cost, which can save both the cost involved in making it as well as the space on the printed circuit board (PCB).

- If you want a sophisticated pulse width modulator which works more accurately and which can have more adjusting capabilities, then it is better to use a microcontroller based pulse width modulator than the one which we are using now.
- However, the circuit or the application for which we are using a pulse width modulator is not so sensitive and hence does not demand so much of accuracy. In such a case, the circuit which we are using with a bare IC 555 is better as it saves our monetary as well as space resources in building the circuit.
- The duty cycle of the circuit can be changed by changing the value of the potentiometer. If we increase the duty cycle, the speed of the motor increases and if we decrease the duty cycle, the speed of the motor decreases.

15

## REFERENCES

1. Gopal K Dubey "Fundamentals of Electric Drives" Narosa Publishing House New Delhi, 1989.

19

2. Muhammad H. Rashid, "Power Electronics Circuits, Devices, and Applications," Prentice Hall, 3rd edition, 2003.



3. <sup>1</sup> Kumara MKSC, Dayananda PRD, Gunatillaka MDPR, Jayawickrama SS, “PC based speed controlling of a dc motor”, A final year report University of Moratuwa Illiniaus USA, 2001102.

4. <sup>1</sup> J Nicolai and T Castagnet , “A Flexible Micro controller Based Chopper Driving a Permanent Magnet DC Motor”, The European Power Electronics Application. 1993

5. A Khoei Kh. Hadidi, “MicroProcessor Based Closed- Loop Speed Control System for DC Motor Using Power MOSFET”, <sup>21</sup> 3rd IEEE international conference on Electronics, Circuits and Systems( 1996) vol.2, pp.1247-1250.

# SPEED CONTROLLED DC MOTOR

---

## ORIGINALITY REPORT

---

15%

SIMILARITY INDEX

%

INTERNET SOURCES

15%

PUBLICATIONS

%

STUDENT PAPERS

---

## PRIMARY SOURCES

---

1

Y.S. Ettomi, S.B.M. Moor, S.M. Bashi, M.K. Hassan. "Micro controller based adjustable closed-loop dc motor speed controller", Proceedings. Student Conference on Research and Development, 2003. SCORED 2003., 2003  
Publication

---

1%

2

I.G.A.P. Raka Agung, S. Huda, I.W. Arta Wijaya. "Speed control for DC motor with pulse width modulation (PWM) method using infrared remote control based on ATmega16 microcontroller", 2014 International Conference on Smart Green Technology in Electrical and Information Systems (ICSGTEIS), 2014  
Publication

---

1%

3

Mohamed Y. Tarnini. "Microcontroller based PMDC motor control for driving 0.5KW scooter", 2014 16th International Power Electronics and Motion Control Conference and Exposition, 2014  
Publication

---

1%

G. Rajeshkanna. "Modern speed control of

4

separately excited DC Motor by Boost converter fed field control method", 2013 International Conference on Computer Communication and Informatics, 2013

Publication

1%

5

Soumya Debashis Das, Nandita Deb, Gyan Ranjan Biswal, Sovan Das. "High Voltage Aspects of Smart Agriculture through GIS Towards Smarter IoT", 2019 International Conference on Automation, Computational and Technology Management (ICACTM), 2019

Publication

1%

6

Alfredo Arnaud, Carlos Galup-Montoro. "A fully integrated physical activity sensing circuit for implantable pacemakers", Proceedings of the 17th symposium on Integrated circuits and system design - SBCCI '04, 2004

Publication

1%

7

"Development of Ingenious Floor Cleaner using ARDUINO", International Journal of Recent Technology and Engineering, 2019

Publication

1%

8

Mahadev S Patil, S P Patil, Devendra N Kyatanavar. "Reversible DC Drive using MOSFET Chopper – A Laboratory Model Development for Undergraduate Students", IETE Journal of Education, 2014

Publication

1%

9

Aryo Nugroho, Darian Rizaludin, Santirianingrum Soebandhi, Lukman Junaedi, Slamet Winardi, Moh Noor Al-Azam. "Automatic Sign of Commencement of Work from Enterprise Resource Planning", 2020 International Conference on Smart Technology and Applications (ICoSTA), 2020

Publication

1%

10

John R. Mick. "Microprogramming for the hardware engineer", ACM SIGMICRO Newsletter, 1976

Publication

1%

11

P. I. Obi, Osita Opua, C. A. Okeke, G. C. Diyoke, I. K. Onwu. "Quantitative Comparison of Direct Current Shunt and Series Motors Speed Control Methods", European Journal of Electrical Engineering and Computer Science, 2018

Publication

1%

12

Josephine, R.L., and S. Suja. "Experimental Investigations with Fuzzy Controller for PV Fed DC Motor Incorporating SEPIC Converter as Efficient Power Interface", Applied Mechanics and Materials, 2014.

Publication

1%

13

"Nanowire Field Effect Transistors: Principles and Applications", Springer Science and

1%

14

"Recent Advancements in System Modelling Applications", Springer Science and Business Media LLC, 2013

Publication

---

<1 %

15

V. Kumar Chinnaiyan, Jovitha Jerome, J. Karpagam, S. Shiek Mohammed. "Design and implementation of high power DC-DC converter and speed control of DC motor using TMS320F240 DSP", 2006 India International Conference on Power Electronics, 2006

Publication

---

<1 %

16

Aung Zaw Latt. "Variable Speed Drive of Single Phase Induction Motor Using Frequency Control Method", 2009 International Conference on Education Technology and Computer, 04/2009

Publication

---

<1 %

17

Brock J. LaMeres. "Chapter 3 Digital Circuitry and Interfacing", Springer Science and Business Media LLC, 2017

Publication

---

<1 %

18

Roshan Kshirsagar, Chetankumar Patil, Ashok Deshpande. "Chapter 24 Development of Environment Friendly Air Conditioner Using Fuzzy logic", Springer Science and Business Media LLC, 2014

<1 %

- 19 Ahmad Al-Diab, Constantinos Sourkounis. <1 %  
"Multi-tracking single-fed PV inverter", Melecon  
2010 - 2010 15th IEEE Mediterranean  
Electrotechnical Conference, 2010

Publication

---

- 20 Yvonne H. Attiyate, Raymond R. Shah. <1 %  
"Chapter  
13 M", Springer Science and Business Media  
LLC, 1992

Publication

---

- 21 N. L. Ismail, K. A. Zakaria, N. S. Moh Nazar, M. <1 %  
Syaripuddin, A. S. N. Mokhtar, S. Thanakodi.  
"DC motor speed control using fuzzy logic  
controller", AIP Publishing, 2018

Publication

---

- 22 Scott. "Signal Control Components", RF <1 %  
Measurements for Cellular Phones and Wireless  
Data Systems, 06/06/2008

Publication

---

- 23 Anguluri Rajasekhar, Shantanu Das, Ajith <1 %  
Abraham. "Fractional Order PID controller  
design for speed control of chopper fed DC  
Motor Drive using Artificial Bee Colony  
algorithm", 2013 World Congress on Nature and  
Biologically Inspired Computing, 2013

Publication

---

---

Exclude quotes      Off

Exclude matches      Off

Exclude bibliography      Off